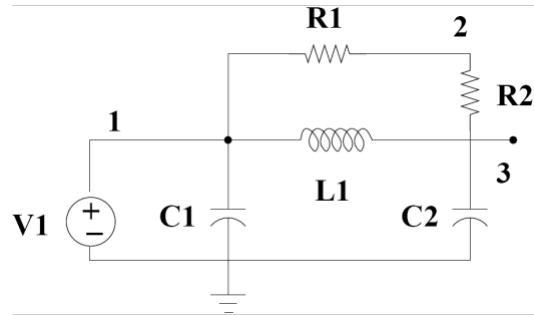


Homework #1


Question 1

Use the element stamp method to build the MNA equations for the following RLC circuit:



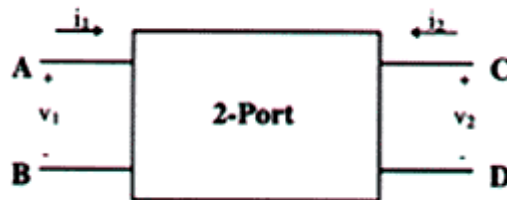Question 2

The 2-port shown below is defined in terms of its h -parameters




The h -parameters are defined as

$$\begin{aligned} v_1 &= h_{11}i_1 + h_{12}v_2 \\ i_2 &= h_{21}i_1 + h_{22}v_2 \end{aligned}$$

- Write the MNA stamp for this element.
- When can a plain nodal analysis be used for this element? Write the nodal stamp.


Question 3

The Boolean switch shown below is controlled by the logic variable L . The switch is closed when $L=1$ and open when $L=0$. Write the MNA stamp that is valid for the switch in both on and off conditions. Note the stamp will be a function of the values of L .

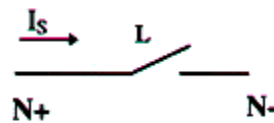

Question 4


Consider a 4-terminal element

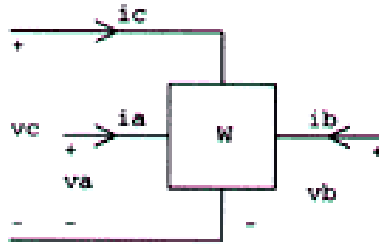

Described by the constitutive relation:

$$\begin{bmatrix} 1 & 0 & 0 \\ 1 & 1 & 0 \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix} + \begin{bmatrix} 1 & 1 & 0 \\ 0 & 1 & -1 \\ 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = 0$$

- Explain why you can *not* use plain nodal analysis for circuits with such an element.
- Using any equation formulation approach you wish, generate the set of equations for the following circuit:

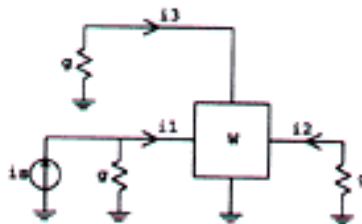

Question 5

Given a RLCM circuit (M here means the mutual inductance) in MNA form,

$$\begin{bmatrix} G + sC & A_l^T \\ -A_l & sL \end{bmatrix} \begin{bmatrix} v_n \\ i_l \end{bmatrix} = \begin{bmatrix} i_n(s) \\ 0 \end{bmatrix}$$

where, G is matrix for resistive components, C is matrix for capacitive elements and L is the matrix for inductive elements. A_l is the incident matrix for inductive branches. $I_n(s)$ is the

independent input current source. \mathbf{v}_n and \mathbf{i}_l is the node voltages and inductive branch current vectors.

- (a) Drive the nodal analysis (NA) formation of the RLCM circuit based on the node reduction formula (Schur decomposition).
- (b) In what condition that the NA formulation is not equivalent to the MNA formulation for the RLCM circuits.